

PROPOSED THEORY

Assume that what is stated below is just a theory and perform experiments (as suggested in the procedure) to test its validity.

In the textbook (section 19-6) it is mentioned that a simple RC circuit can be constructed by connecting a capacitor, a resistor and a battery in series. When the circuit “is closed, current immediately begins to flow through the circuit ... As charge accumulates on the capacitor, the potential difference across it increases ... and the current is reduced until eventually the voltage across the capacitor equals the emf of the battery ... The potential difference across the capacitor ... thus increases in time ... by the formula”

$$V = V_0 \left(1 - e^{-t/RC}\right)$$

When the capacitor is “allowed to discharge through a resistor R ... charge begins to flow ... from one side of the capacitor toward the other side, until it is fully discharged. The voltage across the capacitor decreases” by the exponential formula

$$V = V_0 e^{-t/RC}$$

where V_0 is the initial voltage across the capacitor.